

FUNCTION GENERATOR (F.G.)

that need lower distortion or wider frequency signals.
Within these fields one required other types of generators
would be more appropriate.
Function generator can be used in the development,
test and repair of electronic equipment. For example,
they may be used as a signal source in test equipment
or to introduce an oscillation in a control loop.

a) TRANSISTOR POWER SUPPLY (TPS):-


TPS is designed to provide a stabilized voltage
that can be varied from 0.5 volts at supply current
over 5 range of 1.0 volt to each unit of 0.025 for
line limit of which can be increased by 2 units.
The supply is designed to operate at a temperature
of 0°C to 50°C normal condition is provided for the
unit to an overall ambient, circuit is well insulated
to protection of the circuit elements. Line width
can be less life expectancy is removed or deformed
is decreased from the output terminals. The
circuit can operate on the main supply of 200 V AC
or 220 V & 50 Hz frequently.



c) AUDIO FREQUENCY GENERATOR:-

TRANSISTOR POWER SUPPLY (TPS)

- i) It is a device for producing known and controlling
voltage that stimulate in radio frequency signals.
- A typical audio generator has following parts:
- 1. An oscillator associated with power and
stabilizing a reference level of voltage, power and
stability that provide oscillating for other parts, scaling

Teacher's Signature: _____

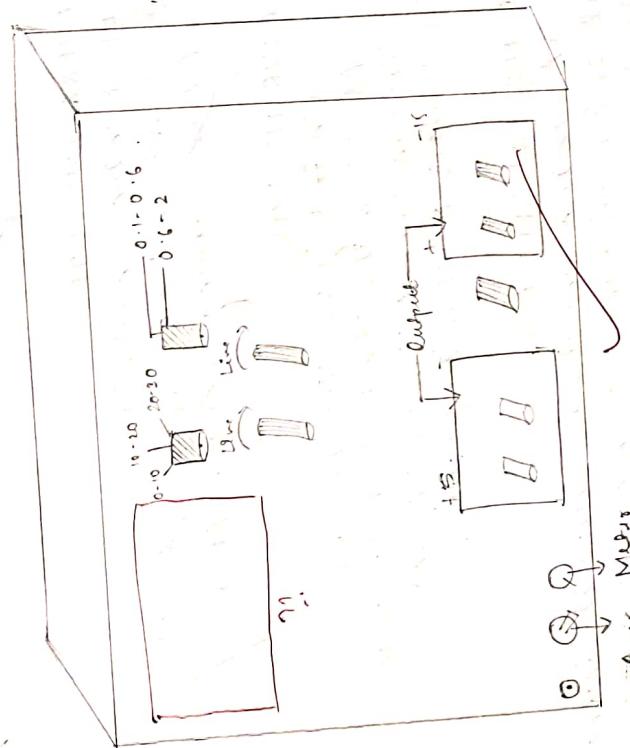

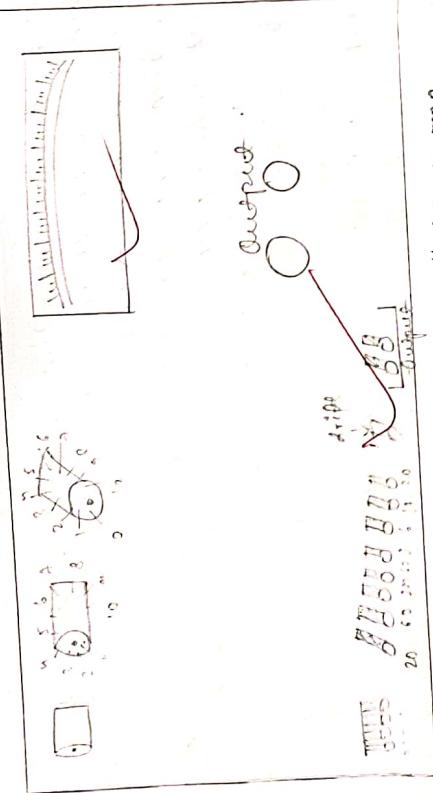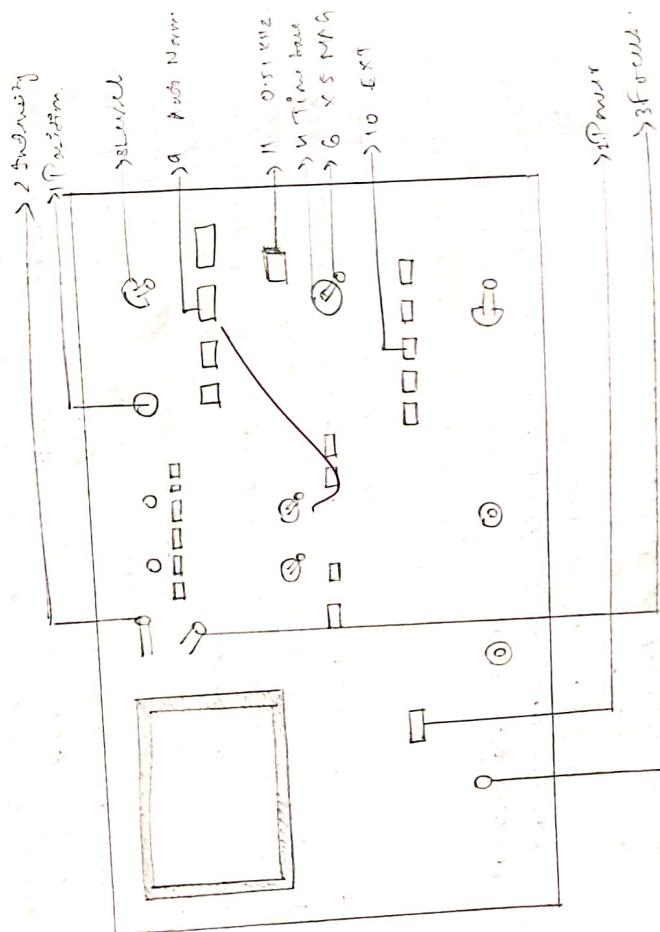AUDIO FREQUENCY GENERATOR

(CATHODE RAY OSCILLATOR)

Setup Part
Variable
Voltage


1. Output terminals an rffactive under test by means of other passing rffg alternator.
2. The principal objection of AFG is the shorting of output terminal of oscillator and an accuracy voltage for audio frequency range of 20 Hz to 20 kHz. In fact, the noise is not removed & signal is not so that voltage introduced into the circuit by feedback from AFG are small and distortion produced is small.

2. a) CATHODE RAY OSCILLOSCOPE
Generally referred to as an electronic 2D a bank of all electrical signals provides a 2-D visual display of the visible wavelength or a screen all owing that one or the other various signal to all of circuit. It is only by using the whole first can correct errors. Unlike in AFG.


- A CRO can be adjusted easily owing to all of its signal and waveform time base set at a fine resolution viewing signal within time of waveform displayed and can provide a number of waveform displayed on the screen simultaneously.


- The vertical deflecting system provides stabilized deflection from point to point on my site has been divided from point to point on the screen several channels. The trigger circuit provides vertical triggering beyond the boundaries of vertical synchronization, calibrated with sweep scales with amplitude 0.01 m/s.

Teacher's Signature:

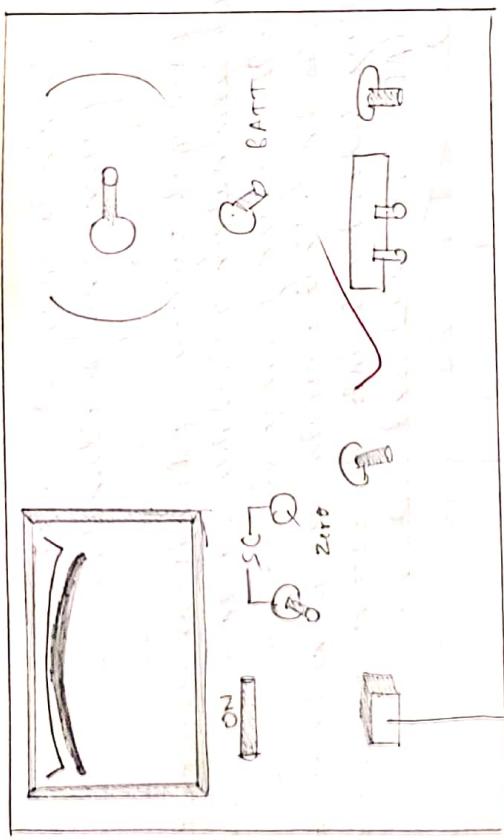


parallel

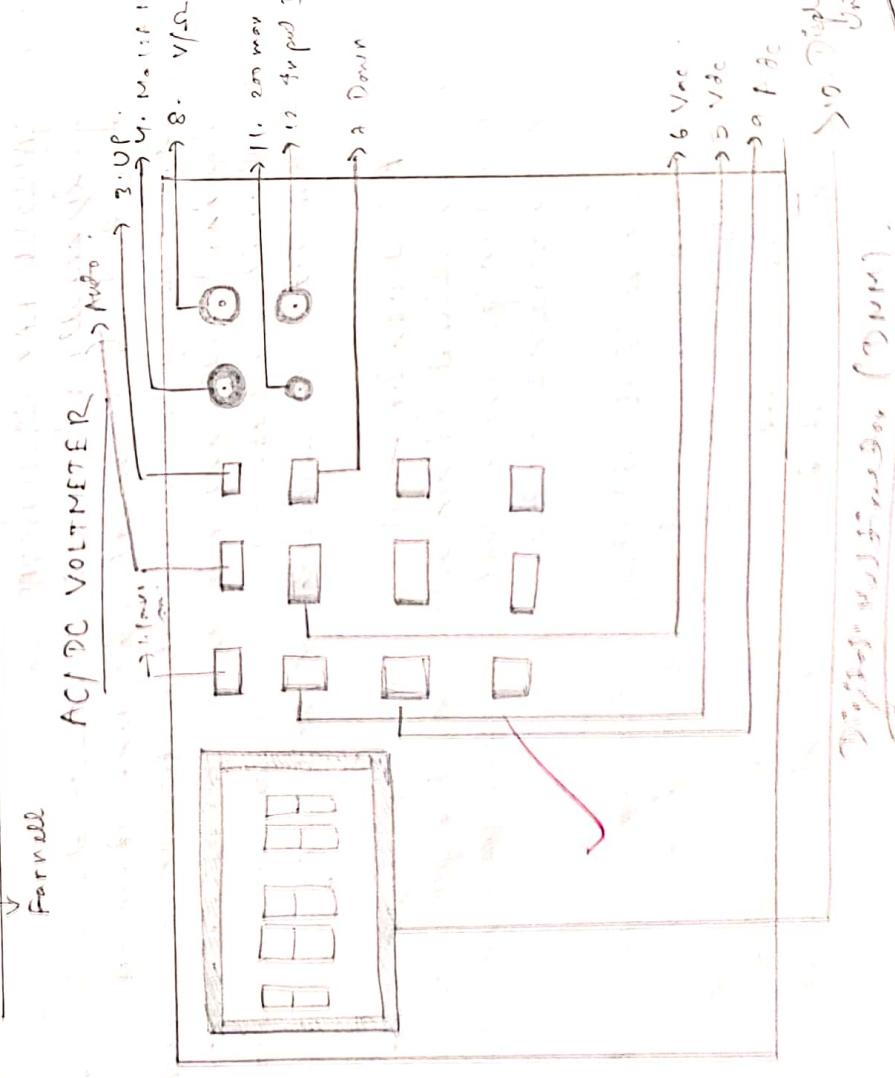


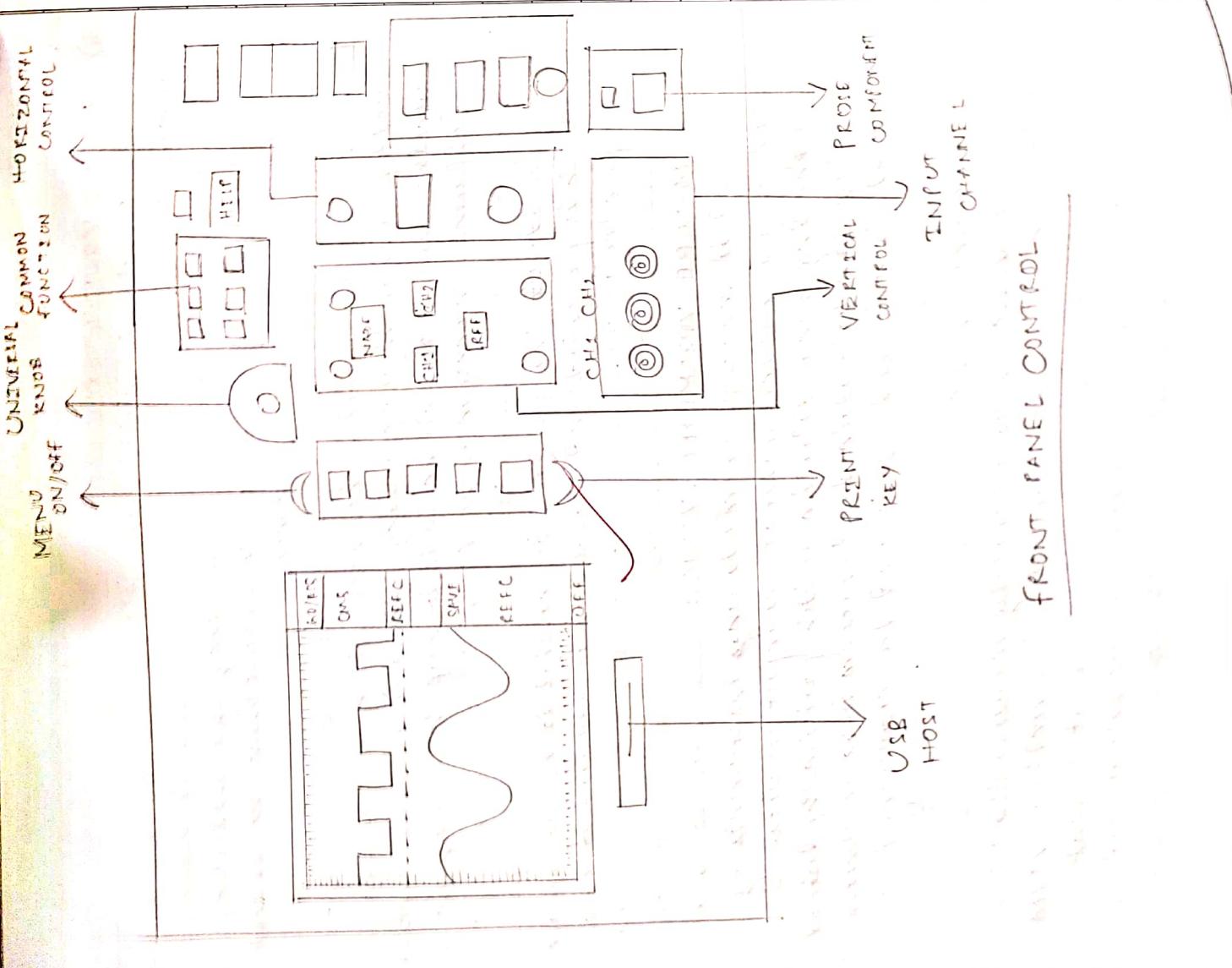


- Capt:** The oscilloscope has stopped acquiring waveform data.
- Autor:** The oscilloscope is in auto mode and is acquiring waveform in the absence of triggers.
- Scan:** The oscilloscope is acquiring and displaying waveform data continuously (in scan mode).
2. Display the position of the present waveform window in longitudinal memory.
 3. Marker shows horizontal trigger position. Turn the HORIZONTAL POSITION control to adjust the marker.
 4. Print key - indicates whether the Print key option is set for print feature or save feature.
 - "Print key" option is set to "Print feature".
 - "Print key" option is set to "Save feature".
 5. Back USB - indicates whether the back USB option is set to USB-TMC or Printer.
 - "Back USB" option is set to "USB-TMC".
 - "Back USB" option is set to "Printer".
 6. Shows the trigger level symbol.
 7. Shows the channel symbol.
 8. Signal coupling symbol.

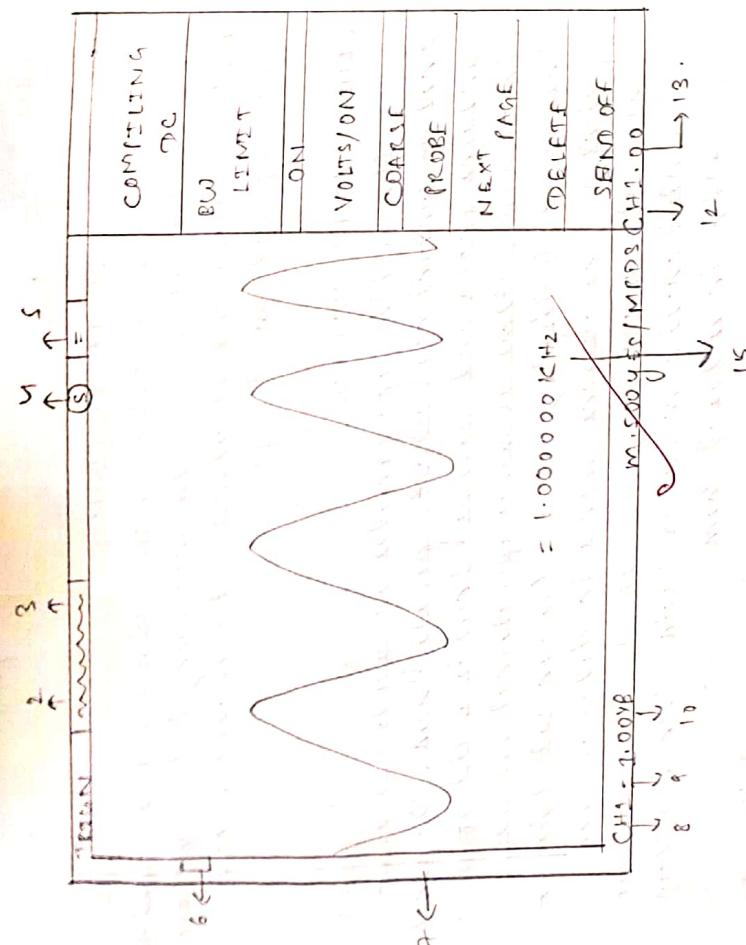


USER DISPLAY INTERFACE

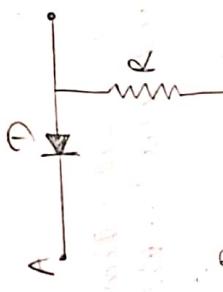


(a) Positive Clipper

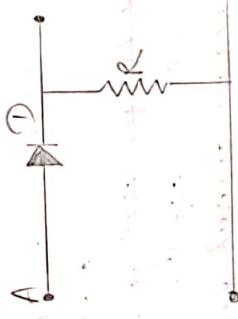

(b) Negative Clipper

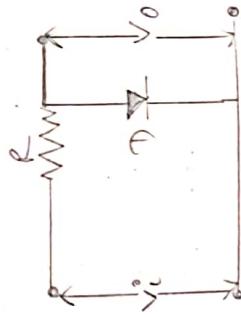

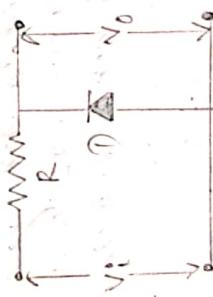(c)
Shunt (parallel) Positive Clipper
Shunt (parallel) Positive Clipp'




(d)
Shunt (parallel) Negative Clipper
Shunt (parallel) Negative Clipp'

$V_{P-P} = 10V$

POSITIVE CLIPPER



Output

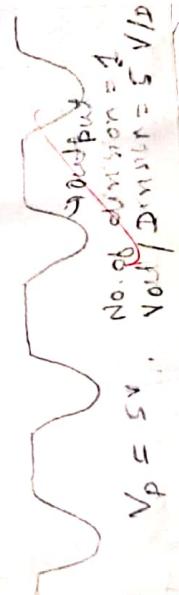


NEGATIVE CLIPPER

No. of $D = 2$

$V_{ID} = 5V$



$V_{P-P} = 10V$


Input

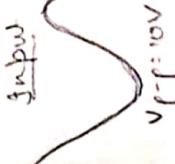

Output



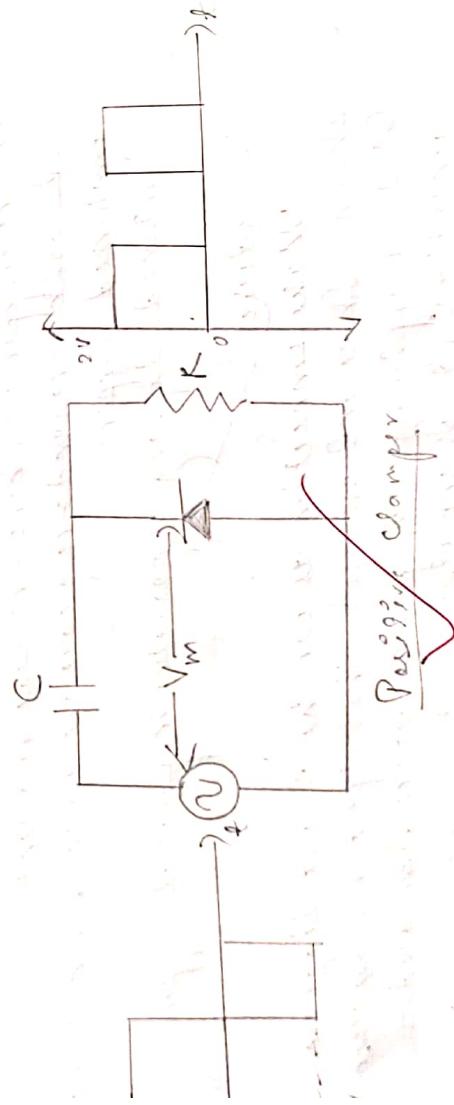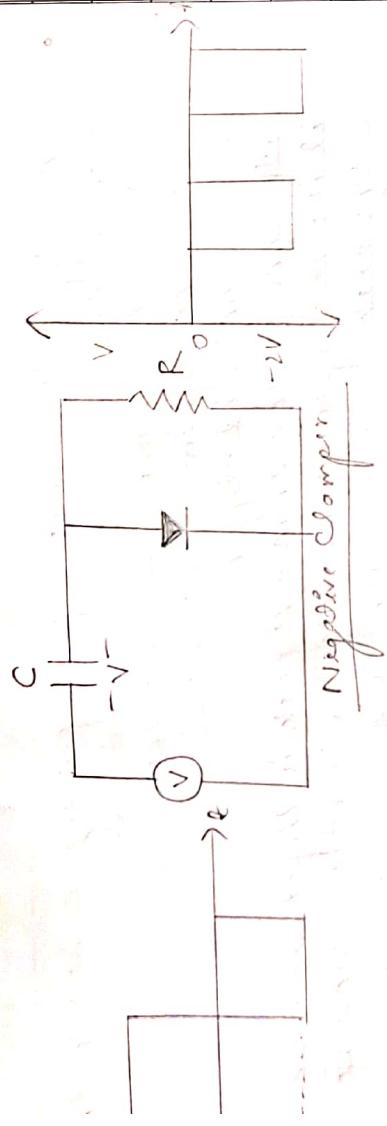

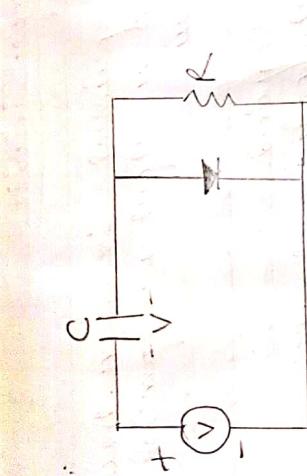


Negative
Clamper

POSITIVE CLAMPER

$$V_{P-P} = 10V$$
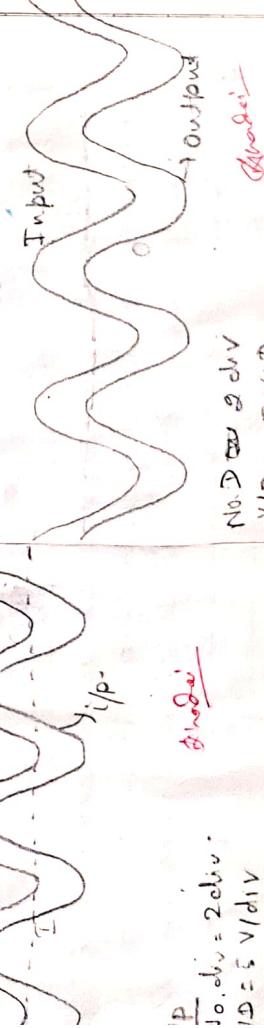
$$\begin{aligned} \text{No. of divisions} &= 5 \\ \text{Voltage per division} &= 2V \end{aligned}$$



$$\begin{aligned} \text{No. of divisions} &= 2 \\ \text{Voltage per division} &= 5V \end{aligned}$$

$$V_{P-P} = 10V$$

*Also See
Diode*

- The magnitude of R and C are so chosen that the time constant $\tau = RC$ should be large enough to insure that the voltage across capacitor does not discharge significantly during the interval, diode is not conducting.

Procedure:

Make connection as per the circuit diagram shown. Trace and measure the output voltage using CRD by applying AC voltage waveform across junction FET of load effect.

Conclusion:

The effect of different input waveform of clamper circuit was observed, traced and measured.

Precaution:

- The connection should be tight.
- Resistance of 1 K ohm is taken.
- The effect of different input waveforms of clamper circuit's output waveform is best observed at 1000 Hz of input waveform.

*Submitted By:
Abhiraj Sharda
Reg. No. - 190516013
Branch - Production
Engineering*

STUDY OF RECTIFIERS**AIM OF THE EXPERIMENT :-**

Study of half-wave, full-wave rectifier with capacitor filter. Record of waveforms, measurement of average rms value and ripples factor.

EQUIPMENTS REQUIRED :-

- 1) CRO (0 - 20 MHz)
- 2) Training model.
- 3) Pace card.

THEORY :-

The process by which an alternating current (or voltage) is converted into a direct current is called **Rectification**.

An electrical device having a low resistance to current in one direction and a relatively high resistance to current in the reverse direction is called a **rectifier**.

HALF WAVE RECTIFIER :-

Since the negative half cycles of input voltage are cut off and at almost constant output load of voltage in the circuit which uses a single diode, the circuit is referred to as a half-wave rectifier.

The process of removing one half of the input signal or establish a DC level is called **half-wave rectification**.

FULL WAVE RECTIFIER :-

When two diodes are so connected that conduction occurs through one diode during one half

Teacher's Signature : _____

of the input voltage cycle, and through the other diode, during the first half of its cycle. A unidirectional current flows through the load resistance during full cycle of its input voltage. Such a circuit is called a full wave rectifier. The D.C. level obtained from a conventional rectifier can be improved to 100 percent using a full wave rectifier and the process is called full-wave rectifier.

CENTRE TAPPED TRANSFORMER: - A transformer having only with two secondaries but requiring a center-tapped secondary to minimize the effect of magnetization of the secondary of the transformer.

PROCEDURE:-

~~Transformer was fitted 220V, 50Hz source was given to primary coil of the transformer and the AC-voltmeter of rat 2000 values were observed without any load at the secondary of the transformer.~~


~~The circuit was connected to the secondary terminal of the transformer.~~

~~CRO was connected across load.~~

~~CRO switch was kept in ground mode and original ratio was observed and observed adjusted as 1:one.~~

~~CRO was switched into 10 mV, and the waveform was observed. Amplitude Vm was noted down and frequency from the screen along with its multiplication factor was also noted down.~~

Teacher's Signature : _____

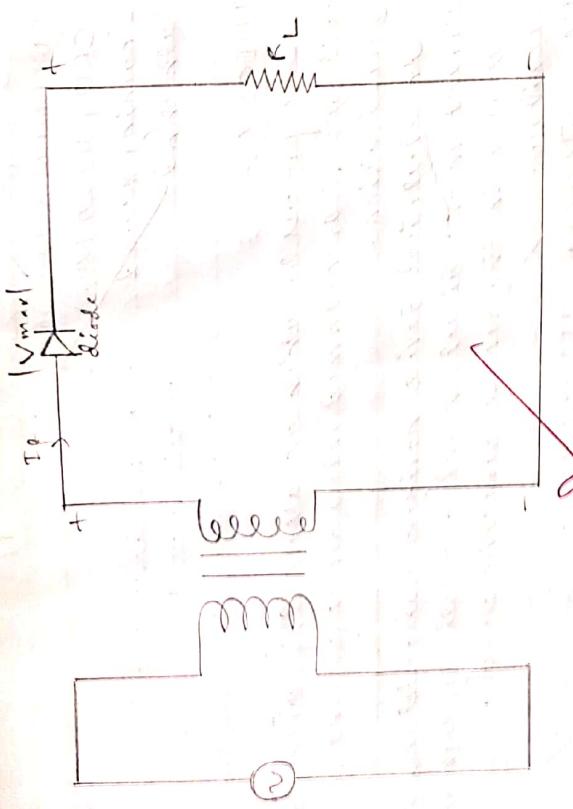

Circuit Diagram of Half-wave Rectifier

Expt. No. 3

Date
Page No. J.M

INPUT WAVEFORM OF FULL WAVE RECTIFIER



$$V_{P-P} = 42.80V$$

OUTPUT WAVEFORM OF FULL WAVE RECTIFIER



$$V_{P-P} = 39.00V$$

• V_{dc} was calculated using the relation :-

$$\begin{aligned} V_{dc} &= V_{rms} (\text{avg.-wave}) \\ V_{dc} &= 2V_{rms} (\text{full-wave}) \end{aligned}$$

- The CRO was connected with AC mode and the waveform was observed. Amplitude, V_{rms} and frequency was varied down from the screen along with the amplitude factor.
- V_{dc} was calculated using the relation :-

$$V_{rms}^2 = V_{dc}^2 + V_{r.m.s}^2$$

$$V_{rms} = V_{dc} / \sqrt{2} (\text{full-wave})$$

$$\begin{aligned} V_{rms} &= V_{dc} / \sqrt{2} (\text{full-wave}) \\ \text{Ripple Factor} &\text{ was calculated from the formula } f = \frac{V_{r.m.s}}{V_{dc}} \end{aligned}$$

CALCULATION :-


• AC-D.C-Wave Rectifier:-

$$\begin{aligned} \text{Input} \quad V_{P-P} &= 7.3V \\ \text{Output} \quad V_{eff} &= 36.80V \end{aligned}$$

$$\begin{aligned} \text{Maximum Ripple, } V_m &= 36.80 / \sqrt{2} \\ V_{rms} &= \frac{V_m}{\sqrt{2}} = 18.4 / \sqrt{2} \\ V_{dc} &= \frac{V_m}{\pi} = 18.4 / \frac{\pi}{2} = 5.25V \end{aligned}$$

$$\begin{aligned} V_{ac} &= \left(V_{rms}^2 - V_{dc}^2 \right)^{\frac{1}{2}} = \sqrt{(18.4)^2 - (5.25)^2} \\ &= \sqrt{341.44 - 27.5625} \\ &= \sqrt{313.8775} = 17.71V \end{aligned}$$

Teacher's Signature :

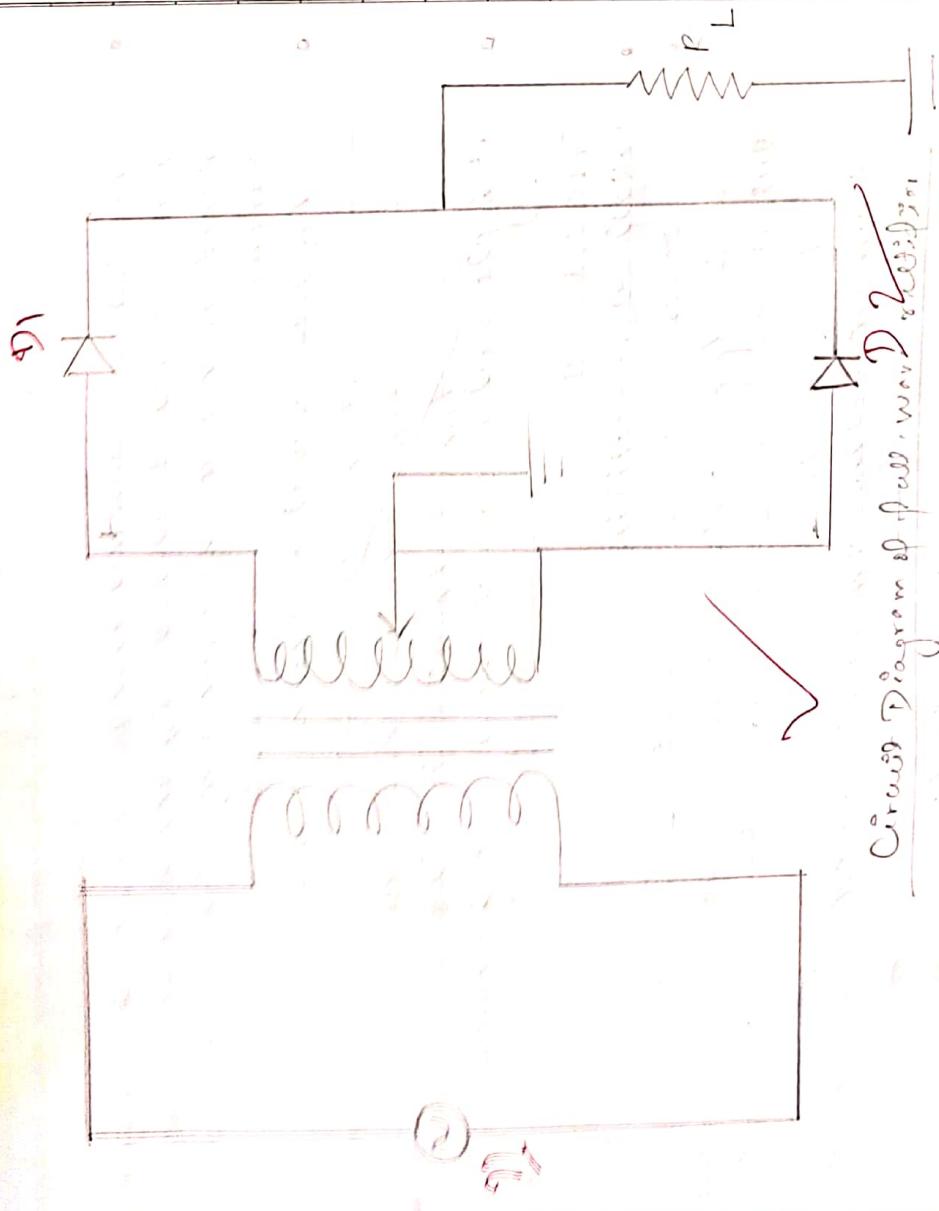

Circuit Diagram of wave D2

CONCLUSION:-

The half-wave and full wave zippers were
sewed with hand sewing machine and were
preserving of zipper in value and zippa
part was recorded.

PRECAUTION:-

- Connections should be avoided unnecessarily.
- But, performance is observed at 50 Hz and 230V.

Ans for
~~Ques 10~~

Submitted by :-
Latika Sharma
Regd.no - 1802116013
Electro-Production Engineering

AIM OF THE EXPERIMENT :-

Digital characteristics of NPN/PNP transistor in common emitter configuration and measure of DC current amplification factor from the graph (α_{TC}/α_{TB}) -

APPARATUS REQUIRED :-

- | QUANTITY | 1 |
|---------------------------------------|---|
| 1. Breadboard or universal breadboard | 1 |
| 2. Transistor power supply (TPS) | 2 |
| 3. DC microammeter | 1 |
| 4. Digital multimeter | 1 |
| 5. Transistor | 1 |
| 6. Resistor (22K, 1K) | 2 |

THEORY :-

The transistor is used to operate in the active region. The microammeter and voltmeter are connected to measure the base current (I_B) and the voltage are used in the base-emitter circuit to measure collector current (I_C) and the voltage between base and emitter. Similarly, voltmeter and voltmeter are connected to collect current in collector circuit & measure collector voltage (V_C).

In this configuration we use emitter as common terminal for both input and output. Here, the input is applied between base emitter terminal. This type of configuration is mostly used in the application of transistor based amplifiers. In this configuration, transistor current is equal to the sum of $[I_e + I_B]$

PROCEDURE:-

- The instruments and components were connected in breadboard as per the circuit diagram by following the proper rules of ix.
- ~~In I_B was set at different values by varying V_{BB}. The DC voltage V_{CE} was applied from T₂ and the interval of 5V or a constant 5V value and it was measured by multimeter.~~
- The A_{Tc} and A_{TB} graph was plotted in the graph and the current and voltage gain was calculated by using the formula (A_{Tc}/A_{TB})

OUTPUT CHARACTERISTICS :-

~~I_O is drawn by taking V_{CE} in Y-axis and T_c in X-axis for different I_B values.~~

NOTE:-

~~For NPN transistor the supplied and meter polarities will be reverse of the above circuit.~~

PRECAUTIONS:-

~~The connection was checked before connecting it on.~~

Scale:


$$X - axis: 1 cm \equiv 1 m$$

$$Y - axis: 1 cm \equiv 1 m$$

Current Amplification factor = 1.1

A.T.C

$$\approx 4.5 - 3.1 = 0$$

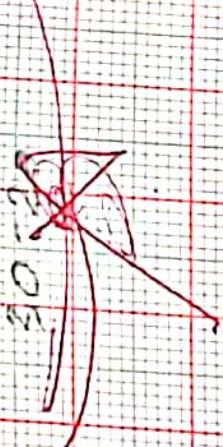

AIM OF THE EXPERIMENT:-

To study the op-amp as an inverting and non-inverting amplifier.

EQUIPMENTS REQUIRED:-

- 1) Op-amp & driver sig. 1
- 2) Audio - Frequency generator. 1
- 3) Decade Resistor box. 1
- 4) CRO 1
- 5) Digital Multimeter 1

THEORY:-

An operational amplifier, or op-amp is a very high gain differential amplifier with high input impedance and low output impedance. Typical uses of op-amps are to provide voltage amplification, changes of configuration, oscillation, filter circuit and many types of microcomputational circuits.


(i) Singe Ended Input:- Input signal is connected to one end (input with ground) which results in an output having the same polarity as the applied input signal. Also, the signal can be given to two inputs with their own polarities.

(ii) Dual Ended (Differential) Input:- Signal is applied at both inputs, with the resulting amplified output in the phase with that applied between the plus and minus input. When separate signals are applied, then


Teacher's Signature : _____

INVERTING AMPLIFIER:-

$$R_o = 10\Omega$$

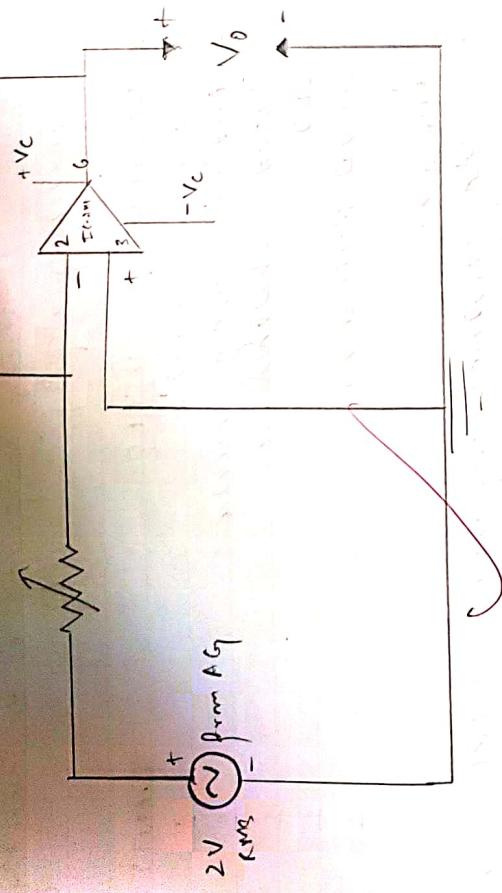

NON-INVERTING AMPLIFIER:-

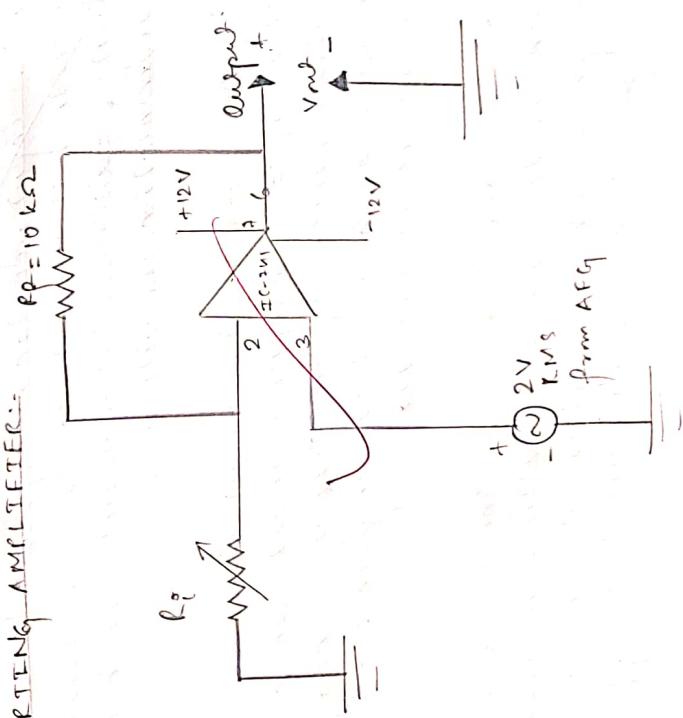

Expt. No. 5

Date.....

Page No. 21.....

Output is the difference $V_1 - V_2$.

(iii) Common Mode Operation: If the same input, the operation is called common mode operation.

The signals that are applied at the input are fully amplified, but the common input signal results in opposite signals at each terminal due to coupling, so the resulting output signal is zero.

- Non-Inverting Amplifier:-

It is more widely used because of its non-invert frequency stability. The voltage across R_f is V_o . Since $V_o > V_i$. This means in general the output voltage across R_f and R_i so that

$$V_o = \frac{(R_f + R_i)}{R_i} V_i$$

$$\Rightarrow \frac{V_o}{V_i} = K_f + K_i = 1 + \frac{R_f}{R_i}$$

- Inverting Amplifier:-

Output is obtained by multiplying the input by a fixed or constant gain, just like the first part of (ii) and feedback voltage (R_f) - this output is then being inverted from the input.

$$V_o = -K_f V_i$$

Teacher's Signature: _____

INVERTING AMPLIFIER

INPUT

$$\text{No of vols/1 div} = 1.4$$

$$V_{P-P} = 1.4 \times 5V$$

$$= 7.0V$$



$$\text{No of vols/1 div} = 1.2$$

$$V_{P-P} = 1.2 \times 5V = 6V$$

NON-INVERTING AMPLIFIER

INPUT

$$\text{No of vols/1 div} = 1.2$$

$$V_{P-P} = 1.2 \times 5V = 6V$$



CALCULATION :-

- In inverting amplifier, $R_f = 10 \text{ k}\Omega$, $R_p = 10 \text{ k}\Omega$
 $V_{in} = 2 \text{ V}$, $V_{out} = -1.92$

$$\text{Experimental gain} = \frac{V_o}{V_i} = \frac{-1.92}{2} = 0.96$$

$$\text{Theoretical gain} = \frac{R_f}{R_p} = \frac{10}{10} = 1$$

- In non-inverting amplifier, $R_f = 10 \text{ k}\Omega$, $R_p = 10 \text{ k}\Omega$
 $V_{in} = 2 \text{ V}$, $V_{out} = 3.96$

~~$$\text{Experimental gain} = \frac{V_o}{V_i} = \frac{3.96}{2} = 1.98$$~~

$$\text{Theoretical gain} = 1 + \frac{R_f}{R_i} = 1 + \frac{10}{10} = 2$$

PRECAUTION :-

- The connection should be right.
- All the connections must be checked before going to the power supply.

CONCLUSION:-

It has been verified that experimental and theoretical gain is almost same.

Submitted by :-
ANKITA ACHARYA

1502110013

PE, N.I.

AIM OF THE EXPERIMENT:-

Verification of truth values for basic logic

gates (AND, OR, NOT, NAND, NOR, EX-OR).

APPARATUS REQUIRED:-

1. Breadboard (1 no).
2. Logic IC Trainer.
3. Jumper wires.
4. Connecting Wires.

THEORY:-

A digital circuit which performs logical operation on one or more inputs. But only one single output is given is called a logic gate. There are different types of logic gates of which a few are given below:

AND gate:-

The AND gate is a logic gate that has two or more inputs but only one output. The output of AND gate is HIGH when all inputs are HIGH. However the output of AND gate is low if any one or all inputs are low.

OR gate:-

An OR gate is a logic gate that has two or more inputs but only one output. The output of OR gate is low if all inputs are low and output is high if any one or all the inputs are HIGH.

AND gate





$$Y = A \cdot B$$





OR gate



NOT gate

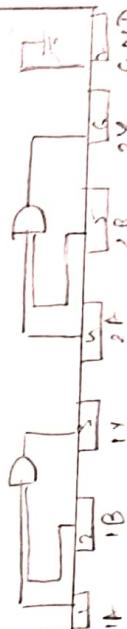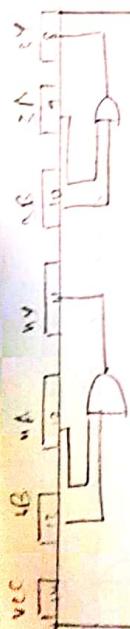

Open collector

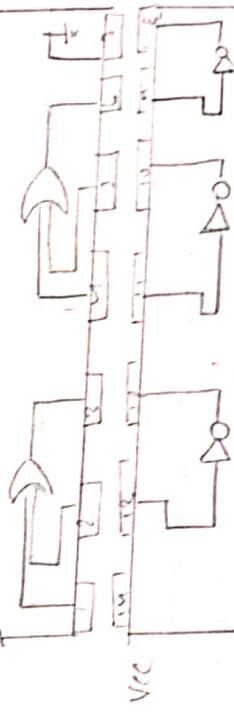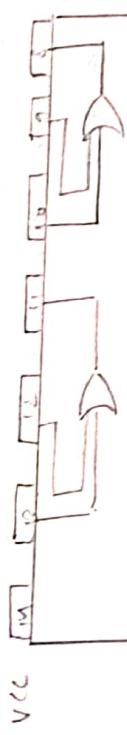

PROCEDURE:-

AND gate:- The Ic Darlington, id. No. 7408 offered. 2-input IC AND gate was identified. The 5V dc from digital IC Arduino was supplied to its IC power pin. +3 Volts for logic '1' and 0' volt for logic '0' was used.
 10 different switches were available. 1 to 10 k ohm ac logic input switches. Any two input pins for IC was chosen and output voltage for the various combination of the input voltage was measured and the results with the truth table of the AND gate was verified.

Table - T.

Gate	Function	Truth Table				Voltage Reading		
		A	B	Y	Output	A	B	Y
AND	$Y = A \text{ AND } B$	0	0	0	0V	0V	0.25V	
	$= A \cdot B$	0	1	0	0V	5V	0.36V	
	$= A \wedge B$	1	0	0	5V	0V	0.25V	
	$= A \vee B$	1	1	1	5V	5V	0.72V	

Table - T.

Gate	Function	Truth Table				Voltage Reading		
		A	B	Y	Output	A	B	Y
OR	$Y = A \text{ OR } B$	0	0	0	0V	0V	0.12V	
	$= A + B$	0	1	1	0V	5V	0.92V	
		1	0	1	5V	0V	3.92V	
		1	1	1	5V	5V	3.92V	

Teacher's Signature: _____

Table III

Gate	Function	Truth Table			
		Input	Output	Voltage	Reading
NOT	$y = \text{NOT } A$	0	1	0V	Y
	$= \bar{A}$	1	0	5V	0.91V

Table - IV

Gate	Function	Truth Table			
		Input	Output	Voltage	Reading
NAND	$y = A \text{ NOT AND } B$	0 0	1	0V	0V
	$= A \text{ NOT AND } B$	0 1	0	5V	5.95V
	$= A \cdot B$	1 0	1	5V	5.91V
	$= A + B$	1 1	0	5V	5.96V
	$= A \oplus B$			5V	0.12V

Table - V

Gate	Function	Truth Table			
		Input	Output	Voltage	Reading
NOE	$y = A \text{ NOT OR } B$	0 0	1	0V	0V
	$= A \text{ NOT OR } B$	0 1	0	5V	0.11V
	$= \overline{A + B}$	1 0	0	5V	0.1mV
	$= A + B$	1 1	1	5V	5V 0.1mV

Table - IV.

Ques	function	Truth table		Voltage scaling	
		Input A	Output Y	Input A	Output Y
Ex:- OR	$y = A \bar{B} + \bar{A}B$	0	0	0	0V
	$= A + \bar{B}$	0	1	1	0.9V
	$= \bar{A}\bar{B} + \bar{A}B$	1	0	1	5V
		1	1	0	0.96V

Conclusion:

From the above given experiment of various gates, we conclude that different gates give right output according to their respective truth table.

Alka Saini
16/11/18

Signed by :-

ANKITA TAKKYA

1802110013

PE

Group - 4

Colour	1 st band	2 nd band	3 rd band	Multiplication	Tolerance
Black	0	0	0	$\times 1\Omega$	$\pm 1\%$
Brown	1	1	1	$\times 10\Omega$	$\pm 2\%$
Red	2	2	2	$\times 100\Omega$	$\pm 1\%$
Orange	3	3	3	$\times 1k\Omega$	$\pm 5\%$
Yellow	4	4	4	$\times 10k\Omega$	$\pm 25\%$
Green	5	5	5	$\times 1M\Omega$	$\pm 10\%$
Blue	6	6	6	$\times 10M\Omega$	$\pm 0.1\%$
Violet	7	7	7	$\times 100M\Omega$	$\pm 0.05\%$
Grey	8	8	8	$\times 1G\Omega$	$\pm 5\%$
White	9	9	9	$\times 10G\Omega$	$\pm 10\%$
Gold					
Silver					

resistance value in hundreds of ohm is expressed in kilo-ohm, i.e. The nominal value of resistor is generally expressed at room temperature of 25°C .

(ii) Tolerance :- Tolerance and accuracy have some meaning. Accuracy is the tolerance by which the value of the resistance is made. Resistors are available with tolerance such as $\pm 10\%$, $\pm 5\%$ in general and more precise with 1% , 0.5% or 0.1% .

(iii) Stability :- A resistor is said to be more stable if its value does not alter from its nominal value. This property is called stability.



Although the carbon composition resistors are less stable, carbon film resistor are fairly stable and metal film and wire wound resistors are most stable.

2. Capacitors:

The capacitors are available in fixed and variable nature. They are classified as:-

- Mica capacitor :- The thickness of mica ranging from 0.15-0.5 mm is placed between the electrodes of copper or lead foil of thickness 0.002 mm.

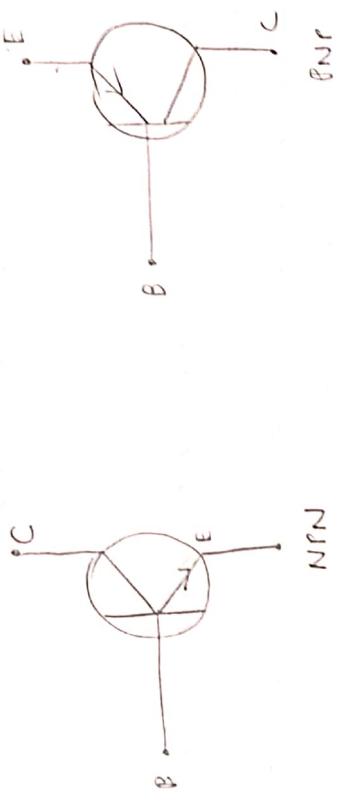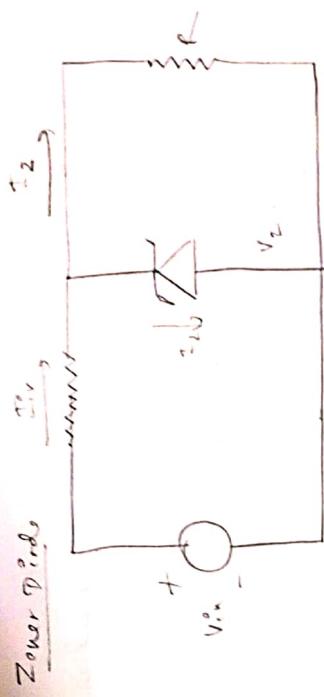- Electrolytic capacitor :- This uses a very thin film of aluminium or lithium oxide as formed by an electrolytic process. Non-polarized capacitors are used in pass, AC, mixer, power supply circuit as well as improvement of power factor in electric circuit. Such capacitors cannot be used in AC circuit and is to be connected with appropriate polarity in DC circuit.



Types of zener diodes:

Observation Table: Measurements of Resistance.

S. no.	Colour Code	Theoretical Value	Experimental Value	% of error
1.	Brown Black, red	$10 \times 10^2 \pm 5\% \Omega$	$0.93 \times 10^3 \Omega$	2%
2.	Gold & Gold			
3.	Brown, green, orange	$15 \times 10^3 \pm 15\% \Omega$	$14.5 \times 10^3 \Omega$	3.14%
4.	Grey, Red, Orange	$8.2 \times 10^3 \pm 10\% \Omega$	$8.0 \times 10^3 \Omega$	2.4%
	Silver			

Measurement of Capacitance.

S. no	Theoretical value (μF)	Experimental Value (μF)	% of error
1.	10	10.48	7.8%
2.	4.7	4.87	3.6%
3.	1	1.07	7%
4.	0.22	0.22	0%

Measurement of Diode Potential:

S. no	Types	Forward Biased	Reverse Biased
1.	Si diode	0.656 V	0.001 V
2.	Zener diode	0.003 V	0.064 V

Determination of Transistor Parameters

S. no	Type	Specifications	V _{BE} (invert)	V _{BE} (forward)
1.	NPN	—	0.003	0.6
2.	NPN	—	0.66	0.6

Teacher's Signature : _____

Expt. No. 7

Date

Page No. 33

Conclusion:-

Now after performing the experiment, we are familiar with various effects of different components and their usage.

Precautions:-

- (i) The colour band of the ruler should be observed carefully.
- (ii) Apparatus range should be set in the multimeter.
- (iii) The base, the pointer and colletor of the galvanometer should be insulated properly.

AIM OF THE EXPERIMENT:-

To study and use of single beam dual trace CRO
to view waveforms and measure rise time, bandwidth, and frequency.

EQUIPMENTS REQUIRED:-


1. CRO (Cathode Ray Oscilloscope)
2. FG (Function Generator)
3. TDS (Tracistor Power Supply)
4. AC millivoltmeter and digital multimeter.

THEORY:-

Cathode Ray Oscilloscope (CRO) is one of the prerequisites of any electronic laboratory and known to be amongst one of the most popular and adaptable instruments. A basic CRO is a test instrument that allows one to "plot" and view two-dimensional (2-D) graphs of electronic signals including voltage, current, phase difference, etc., mainly as a function of time and sometimes as a function of voltage. It has two input channels (vertical channel: V_1 and V_2) along with an in-built X-channel with a knob to set the vertical gradient. The signals that need to be analyzed and studied in detail are fed to any of the two input channels such as the time function available on the X-axis by deflection.

Block Diagram

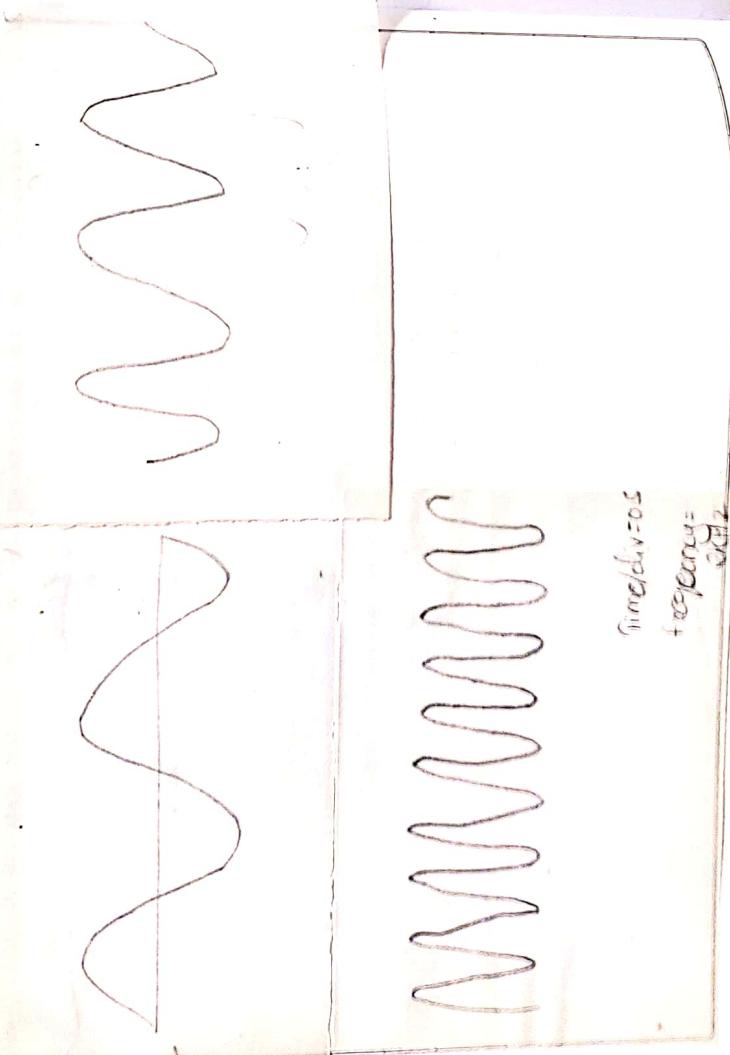- AC voltage measurement
Function generator → Digital multimeter → CRO
- DC voltage measurement
TPS → CRO
- Frequency measurement
Function generator → CRO



Time/div =
1 sec/div =
20 ms

Expt. No. 8

Date

Page No. 24

PROCEDURE

- Measurement of frequency - The function generator was connected to CRO's vertical input terminals. The AC voltage was measured. The frequency (f_1 - CH1) was calculated for 2 kHz and 5 kHz.
- Measurement of AC voltage - The AC voltage was set from ACV 1 V and the voltage was measured from CRO. Similarly, it was measured for 2V and 5V.
- Measurement of DC voltage - The DC voltage was set to 10V, 20V and 30V and the voltage was measured from CRO.

TABULATION:-

Measurement of frequency .

S. No.	Input frequency from ACV in Hz (f ₁)	No. of division X-scale (a)	Time period T (in ms)	Total time t (in ms)	$\frac{t}{T} \times 100\%$
1	1	1	2	0.5	1 0 %
2	2	2	1	0.5	0.5 0 %
3	5	5	1	0.2	5 0 %

Teacher's Signature : _____

Measurement of AC voltage

Sl.no	Voltage from Fig (inverter)	No of division in Y-couln(a)	Value of B (in volt)	Scale B	Result (V/F2) or m	% of error
1	2	3	2	6	2.12	6 %
2	0.95	3	1	3	1.06	11 %
3	0.8	3	1	3	1.06	13 %

Measurement of DC voltage

Sl.no	Input voltage from PS (invert)	No of division in Y-couln(a)	Value of B (a)	Total result (a+b)	% of error
1	10	1	10	10	0 %
2	20	2	10	20	0 %
3	30	3	10	30	0 %

Proceedings:

- (i) The instrument is carefully handled
- (ii) The wire is properly connected
- (iii) The connection is properly checked.

Conclusion:

Using the CEO and offers provided we checked and found the AC voltage, DC voltage and frequency. The CEO has been properly selected and used. Submitted by:- Ankita Acharya

18D2110013

Teacher's Signature : _____

CHARACTERISTIC DIODE.

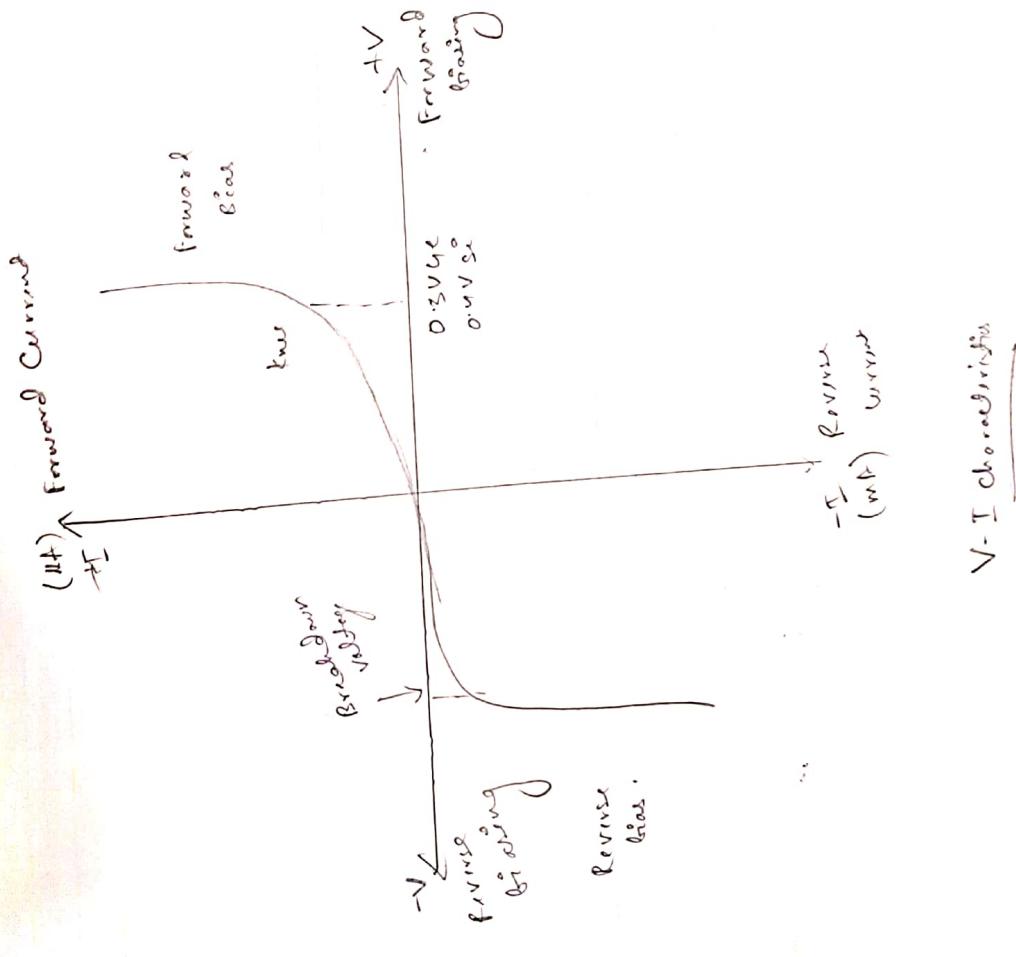
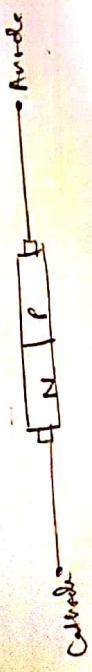


Table of Data:

Sl.no	Input Voltage V _d	Output Voltage V _o (mV)	Diode Bias.			
			V _d = 1.0	V _d = 0.9	V _d = 0.8	V _d = 0.7
1.	0.1	0.152	0	1	1.0	1.029
2.	0.2	0.27	0	2	2.0	2.074
3.	0.3	0.37	0	3	3.0	3.121
4.	0.4	0.43	0.05	4	4.0	4.121
5.	0.5	0.47	0.1	5	5.0	5.110
6.	0.6	0.5	0.2	6	6.0	6.115
7.	0.7	0.513	0.3	7	7.0	7.115
8.	0.8	0.53	0.5	8	8.0	8.115
9.	0.9	0.554	0.6	9	9.0	9.115
10.	1.0	0.548	0.7	10	10.0	10.112
11.	1.1	0.556	0.8	11	11.0	11.115
12.	1.2	0.563	0.9	12	12.0	12.110
13.	1.3	0.570	1.0	13	13.0	13.115
14.	1.4	0.575	1.2	14	14.0	14.20
15.	1.5	0.566	1.3	15	15.0	15.22

Precautions:-

- All connections should be properly clamped.
- Always connect voltmeter in parallel and ammeter in series.
- All connections should be tight enough.

Conclusion:-

The knee voltage of semi-diode was found to be 0.7V

Submitted By:-
Amita Acharya
1802110013

Teacher's Signature _____